

FIFO

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FI_FO is
  Port (
    DATA : in STD_LOGIC_VECTOR(7 downto 0);
    CLK : in STD_LOGIC;
    RST : in STD_LOGIC;
    EN : in STD_LOGIC;
    W : in STD_LOGIC;
    RED : out STD_LOGIC;
    DATAOUT : out STD_LOGIC_VECTOR(7 downto 0)
  );
end FI_FO;
```

architecture Behavioral of FI_FO is


```
  signal WPTR, RPTR : integer range 0 to 15 := 0;
  type FIFO is array (0 to 15) of STD_LOGIC_VECTOR(7 downto 0);
  signal MEM : FIFO;
begin
  process (CLK, RST)
  begin
    if RST = '1' then
      WPTR <= 0;
      RPTR <= 0;
      RED <= '0';
```

```

elsif rising_edge(CLK) then
    if EN = '1' then
        if W = '1' then
            if WPTR < 15 then
                MEM(WPTR) <= DATA;
                WPTR <= WPTR + 1;
            else
                RED <= '1';
            end if;
        else
            if RPTR < WPTR then
                RED <= '0';
                DATAOUT <= MEM(RPTR);
                RPTR <= RPTR + 1;
            else
                RED <= '1';
                DATAOUT <= "00000000";
            end if;
        end if;
    end if;
end if;
end process;
end Behavioral;

```

RTL Schematic:

 

Output:

