

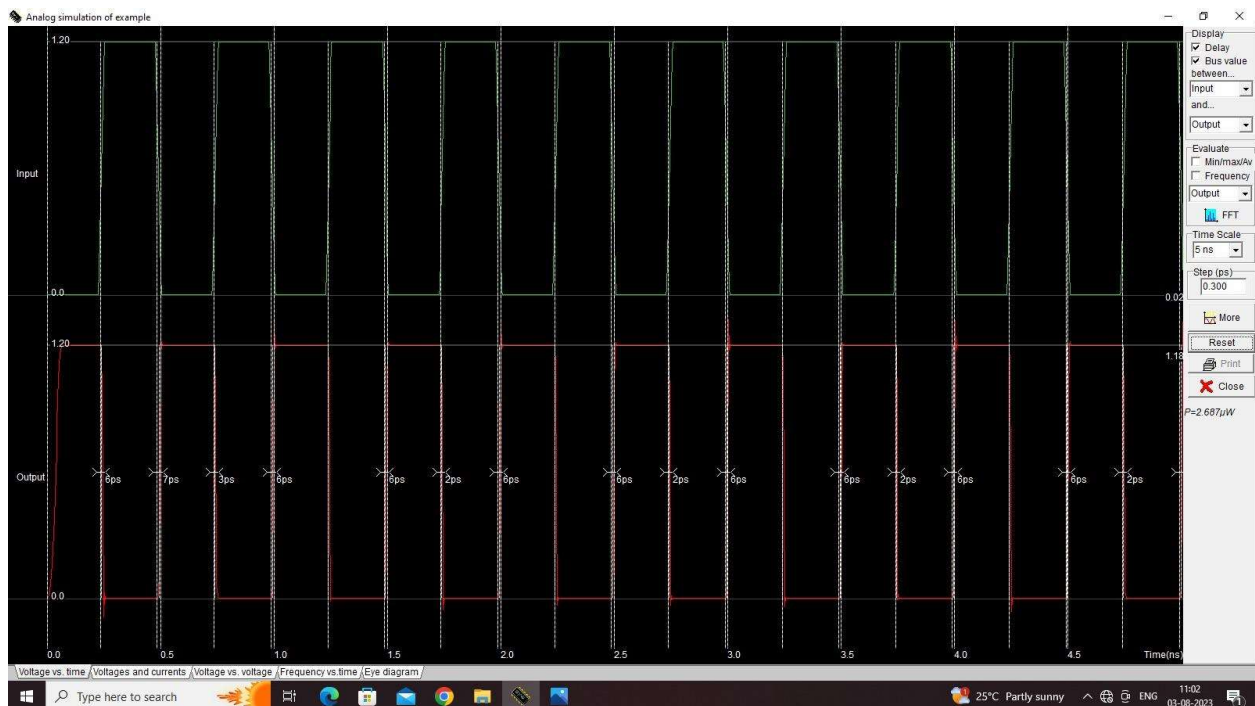


Experiment No:2a



CMOS Inverter Without using capacitor

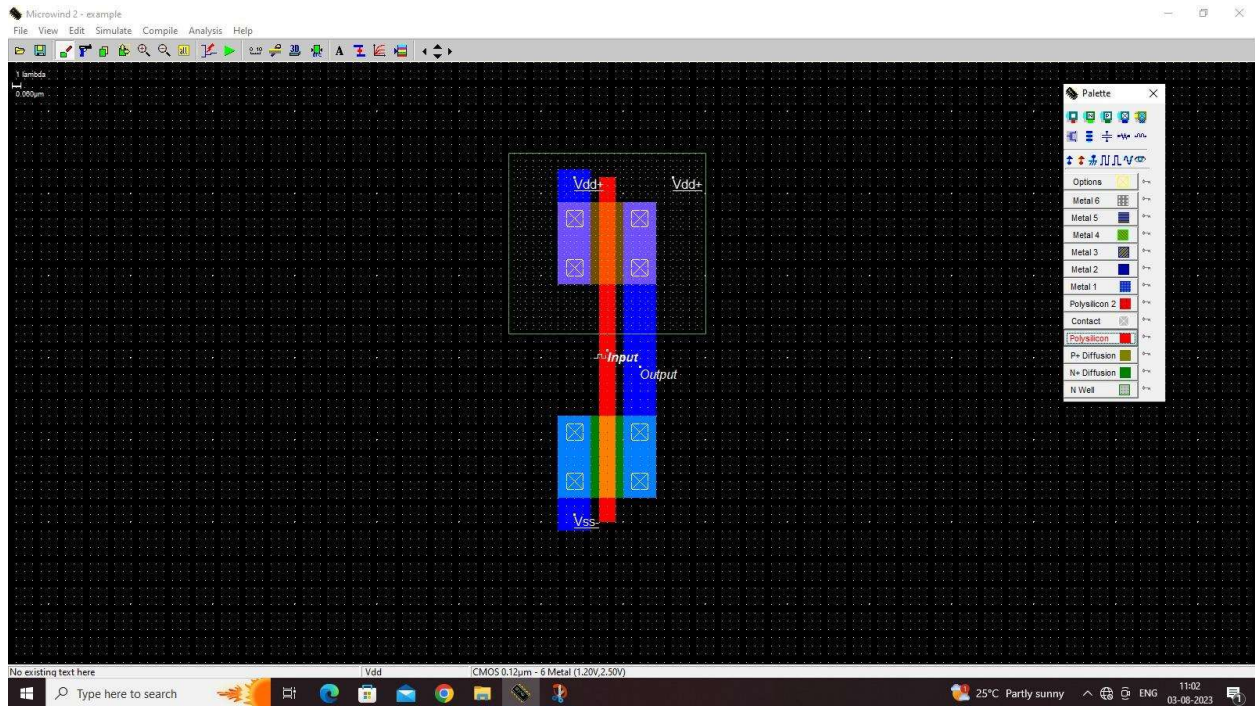

0.001 pF

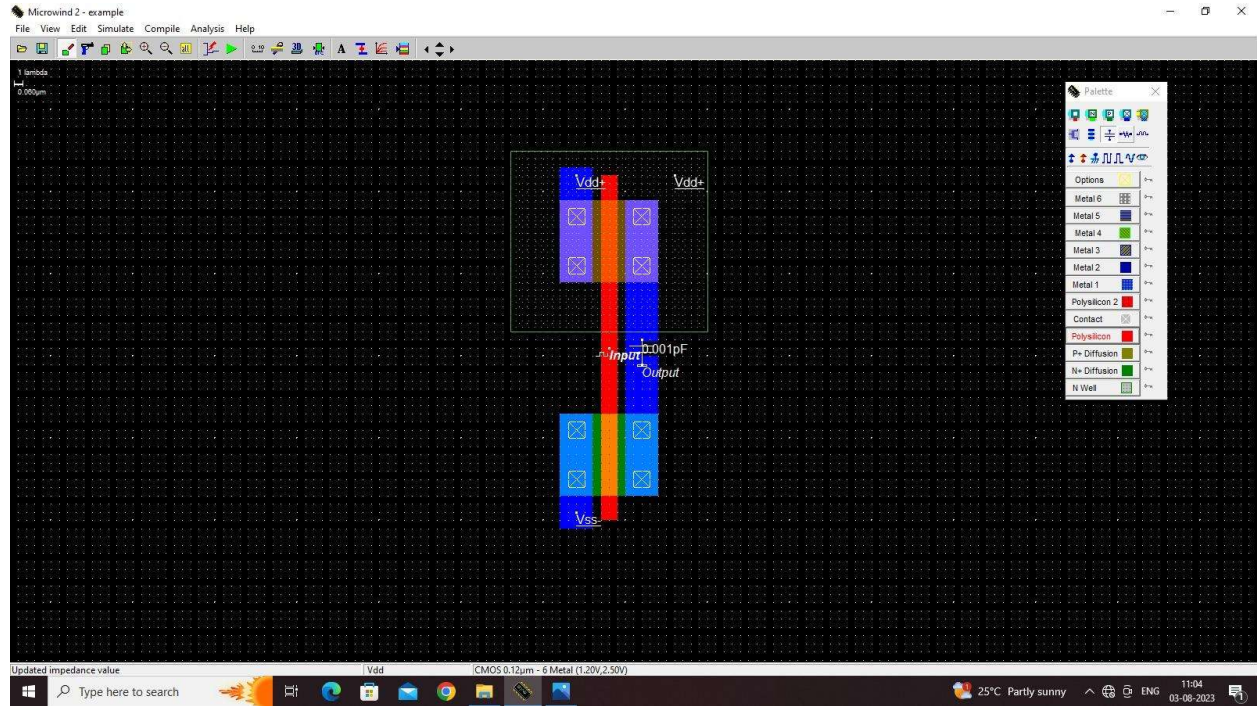

0.01 pF

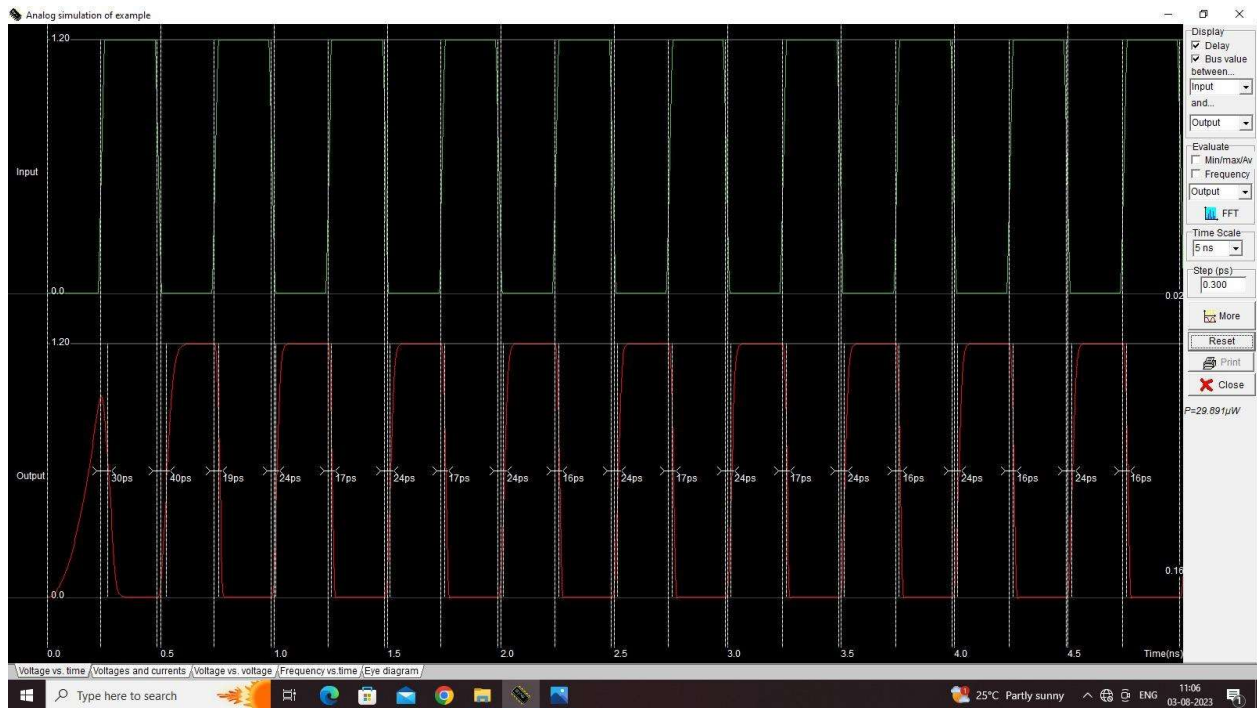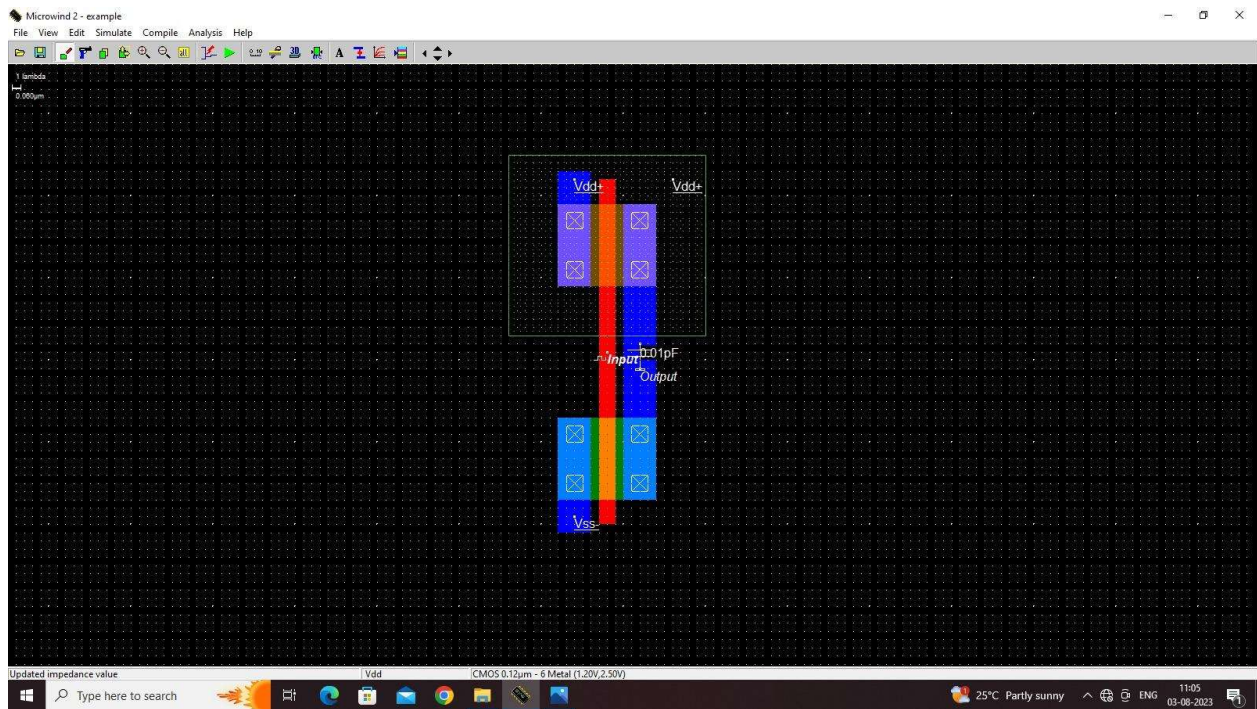

0.1 pF

